

ELEC0014 - Introduction to power and energy systems

The “per unit” system

Thierry Van Cutsem

`t.vancutsem@ulg.ac.be`

`www.montefiore.ulg.ac.be/~vct`

October 2019

Principle

$$\frac{\text{value of a quantity in physical unit}}{\text{value of corresponding "base" in same unit}} = \text{value of quantity in per unit (pu)}$$

Advantages:

- the parameters of devices with similar design have close values in per unit, whatever the power of the device, **provided they are referred to that power**
 - ⇒ check of data validity is easier
 - ⇒ default values can be substituted to unavailable parameters
- in normal operating conditions, voltages in per unit are close to one
 - ⇒ better conditioning of numerical computations
- the ideal transformer present in the model of a real transformer disappears after converting the parameters in per unit.

Example

It is known that the internal reactance of a synchronous machine lies typically in the range [1.5 2.5] pu (on the machine base)

- A machine with the characteristics (20 kV, 300 MVA) has a reactance of 2.667 Ω . Is this a normal value ?

*We will see that the base impedance is $20^2/300 = 1.333 \Omega$
value of reactance in per unit = $2.667/1.333 = 2 pu$
 \Rightarrow quite normal value !*

- Same question for a machine with the characteristics (15 kV, 30 MVA)

*The base impedance is now $15^2/30 = 7.5 \Omega$
value of reactance in per unit = $2.667/7.5 = 0.356 pu$
 \Rightarrow abnormal small value !*

Converting a simple circuit in per unit

Converting an electric circuit in per unit \implies choosing 3 base quantities

for instance: power S_B voltage V_B time t_B

The other base values are obtained using fundamental laws of Electricity:

$$\text{base current: } I_B = \frac{S_B}{V_B}$$

$$\text{base impedance: } Z_B = \frac{V_B}{I_B} = \frac{V_B^2}{S_B}$$

$$\text{base magnetic flux: } \psi_B = V_B t_B$$

$$\text{base inductance: } L_B = \frac{\psi_B}{I_B} = \frac{V_B^2 t_B}{S_B}$$

$$\text{base angular frequency: } \omega_B = \frac{Z_B}{L_B} = \frac{1}{t_B}$$

V_B, I_B : RMS values.

Variant (adopted in this course)

Consider an AC circuit operating at frequency f_N .

Choosing a base angular frequency instead of a base time:

$$\omega_B = \omega_N = 2\pi f_N \quad \text{rad/s}$$

from which one derives:

$$t_B = \frac{1}{\omega_B} = \frac{1}{\omega_N} = \frac{1}{2\pi f_N} \quad \text{s}$$

With this choice:

$$X_{pu} = \frac{X}{Z_B} = \frac{\omega_N L}{\omega_B L_B} = \frac{L}{L_B} = L_{pu}$$

At frequency f_N , the reactance and the inductance have the same per unit value!

Converting in per unit a typical sinusoidal relation

In MVA, MW and Mvar:

$$S = V I \cos(\theta - \psi) + j V I \sin(\theta - \psi)$$

In per unit:

$$\begin{aligned} S_{pu} &= \frac{S}{S_B} = \frac{V I}{V_B I_B} \cos(\theta - \psi) + j \frac{V I}{V_B I_B} \sin(\theta - \psi) \\ &= V_{pu} I_{pu} \cos(\theta - \psi) + j V_{pu} I_{pu} \sin(\theta - \psi) \end{aligned}$$

Same equation in physical units and in per unit !

In the above steady-state equation, time does not appear explicitly. Hence, only S_B and V_B are used.

Converting in per unit a typical dynamic equation

In volts:

$$v = R i + L \frac{d i}{d t}$$

In per unit:

$$v_{pu} = \frac{v}{V_B} = \frac{R i}{Z_B I_B} + \frac{L}{\omega_B L_B I_B} \frac{d i}{d t} = R_{pu} i_{pu} + L_{pu} \frac{1}{\omega_B} \frac{d i_{pu}}{d t} = R_{pu} i_{pu} + L_{pu} \frac{d i_{pu}}{d t_{pu}}$$

In the above equation, time appears explicitly. There are two options:

- all variables, including time, are converted in per unit
 → identical equations in physical units and in per unit
- time is kept in seconds
 → there appears a factor $1/\omega_B$ in front of the derivation operator.

Converting in per unit two magnetically coupled circuits

Flux-current relations:

$$\psi_1 = L_{11}i_1 + L_{12}i_2$$

$$\psi_2 = L_{21}i_1 + L_{22}i_2$$

Identical times. For reasons of simplicity we take: $t_{1B} = t_{2B}$

Symmetry of inductance matrices. In Henry, one has: $L_{12} = L_{21}$. We want that this property still holds true in per unit.

$$\begin{aligned} \psi_{1pu} = \frac{\psi_1}{\psi_{1B}} &= \frac{L_{11}}{L_{1B}} \frac{i_1}{I_{1B}} + \frac{L_{12}}{L_{1B}} \frac{i_2}{I_{1B}} = L_{11pu}i_{1pu} + \underbrace{\frac{L_{12}I_{2B}}{L_{1B}I_{1B}}}_{= L_{12pu}} i_{2pu} \end{aligned}$$

Similarly for the second circuit: $L_{21pu} = \frac{L_{21}I_{1B}}{L_{2B}I_{2B}}$

$$L_{12pu} = L_{21pu} \Leftrightarrow \frac{I_{2B}}{L_{1B}I_{1B}} = \frac{I_{1B}}{L_{2B}I_{2B}} \Leftrightarrow S_{1B} t_{1B} = S_{2B} t_{2B} \Leftrightarrow S_{1B} = S_{2B}$$

A per unit system preserving symmetry of inductance matrices is called *reciprocal*.

Summary

circuit # 1	circuit # 2	
S_B	S_B	← one degree of freedom
t_B	t_B	= $1/\omega_N$
V_{1B}	V_{2B}	← one degree of freedom in each circuit

Application to a network including several voltage levels connected through transformers:

- the same base power S_B is taken at all voltage levels.
Usual value in transmission systems: 100 MVA
- the same base time t_B is taken everywhere (not used in steady state)
- at each voltage level, the base voltage is chosen in relation with the nominal voltage of the equipment.

Converting in per unit a three-phase circuit

- Same base time t_B and same base power S_B everywhere
- at each voltage level, a base V_B is chosen for all phase-to-neutral voltages.

1st case. Unbalanced operation - analysis of the three phases

Convenient choice: $S_B =$ **single-phase** power

$$\rightarrow \text{base current: } I_B = \frac{S_B}{V_B}$$

$$\rightarrow \text{base impedance: } Z_B = \frac{V_B}{I_B} = \frac{V_B^2}{S_B} \quad \text{etc.}$$

Example. Convert in per unit the expression of the three-phase complex power:

$$S = \bar{V}_a \bar{I}_a^* + \bar{V}_b \bar{I}_b^* + \bar{V}_c \bar{I}_c^*$$

$$S_{pu} = \frac{S}{S_B} = \frac{\bar{V}_a}{V_B} \frac{\bar{I}_a^*}{I_B} + \frac{\bar{V}_b}{V_B} \frac{\bar{I}_b^*}{I_B} + \frac{\bar{V}_c}{V_B} \frac{\bar{I}_c^*}{I_B} = \bar{V}_{a\ pu} \bar{I}_{a\ pu}^* + \bar{V}_{b\ pu} \bar{I}_{b\ pu}^* + \bar{V}_{c\ pu} \bar{I}_{c\ pu}^*$$

Identical expressions in physical units and in per unit !

2nd case. Balanced operation - per phase analysis

Convenient choice: $S_B =$ **three-phase** power

$$\rightarrow \text{base current: } I_B = \frac{S_B}{3V_B} = \frac{S_B}{\sqrt{3}U_B} \quad U_B = \sqrt{3}V_B$$

$$\rightarrow \text{base impedance: } Z_B = \frac{V_B}{I_B} = \frac{3V_B^2}{S_B} = \frac{U_B^2}{S_B} \quad \text{etc.}$$

Example. Convert in per unit the expression of the three-phase complex power:

$$S = \bar{V}_a \bar{I}_a^* + \bar{V}_b \bar{I}_b^* + \bar{V}_c \bar{I}_c^* = 3 \bar{V}_a \bar{I}_a^*$$

$$S_{pu} = \frac{S}{S_B} = \frac{3 \bar{V}_a \bar{I}_a^*}{3 V_B I_B} = \bar{V}_{a\,pu} \bar{I}_{a\,pu}^*$$

- ① All calculations are performed in a single phase, and in per unit
- ② at the end, the power in all three phases is obtained by multiplying the power in per unit by S_B .

Change of base

In a three-phase circuit, an impedance Z (in ohm) becomes in per unit

in the first base:
$$Z_{pu1} = \frac{Z}{Z_{B1}} = \frac{Z S_{B1}}{3V_{B1}^2}$$

in the second base:
$$Z_{pu2} = \frac{Z}{Z_{B2}} = \frac{Z S_{B2}}{3V_{B2}^2}$$

Hence the formula to change from the first to the second base is:

$$Z_{pu2} = Z_{pu1} \frac{S_{B2}}{S_{B1}} \left(\frac{V_{B1}}{V_{B2}} \right)^2$$